

Seat No.	
----------	--

B.Sc. (Part - I) (Semester - I) Examination, November-2018**ELECTRONICS****Basic Electronics (Paper - I)****Sub. Code : 59666****Day and Date : Saturday, 24 - 11 - 2018****Total Marks : 50****Time : 12.00 noon to 2.00 p.m.**

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicate full marks.
 - 3) Draw neat diagrams wherever necessary.
 - 4) Use of log table and calculator is allowed.

Q1) Select most correct alternatives of the following: [10]

- a) The resistor having colour bands sequence Green, violet and Orange has the resistance Value.
- | | |
|----------|----------|
| i) 57 | ii) 570 |
| iii) 5.7 | iv) 57 k |
- b) Which of the following is passive circuit element _____
- | | |
|---------------|------------------|
| i) Resistor | ii) Capacitor |
| iii) Inductor | iv) All of these |
- c) Electromagnetic switch is _____
- | | |
|-----------|-----------|
| i) SPST | ii) SPDT |
| iii) DPDT | iv) Relay |
- d) Voltage division rule is applicable to _____ circuit.
- | | |
|-------------|-------------------|
| i) Ladder | ii) Parallel |
| iii) Series | iv) None of these |

P.T.O.

[20]

- Give the classification of Capacitors, Explain construction and working of, Aluminium Electrolytic Capacitor.
- State and explain Kirchhoff's Voltage and Current Laws.
- Explain Fleming's right hand rule. Determine the magnitude of induced e.m.f. in a conductor placed in magnetic field.

Q3) Attempt any four of the following.

- Give the construction and working of wire wound potentiometer.
- State principle of transformer, what do you mean by step up and step down-transformer.
- Give construction and working of electromagnetic relay.
- Explain Mesh analysis method for DC resistive Circuit.
- Explain Coulomb's Law in Magnetism.
- For the circuit shown in figure find the value of R_L for maximum power transfer. Also find the value of this maximum power.

